

CPU Datapaths 1

CS 154: Computer Architecture

Lecture #11

Winter 2020

Ziad Matni, Ph.D.

Dept. of Computer Science, UCSB


Administrative

- Exam grades will be announced by the weekend
- New lab this week (Lab 6)

Lecture Outline


- Logic Design Refresher
- Datapaths

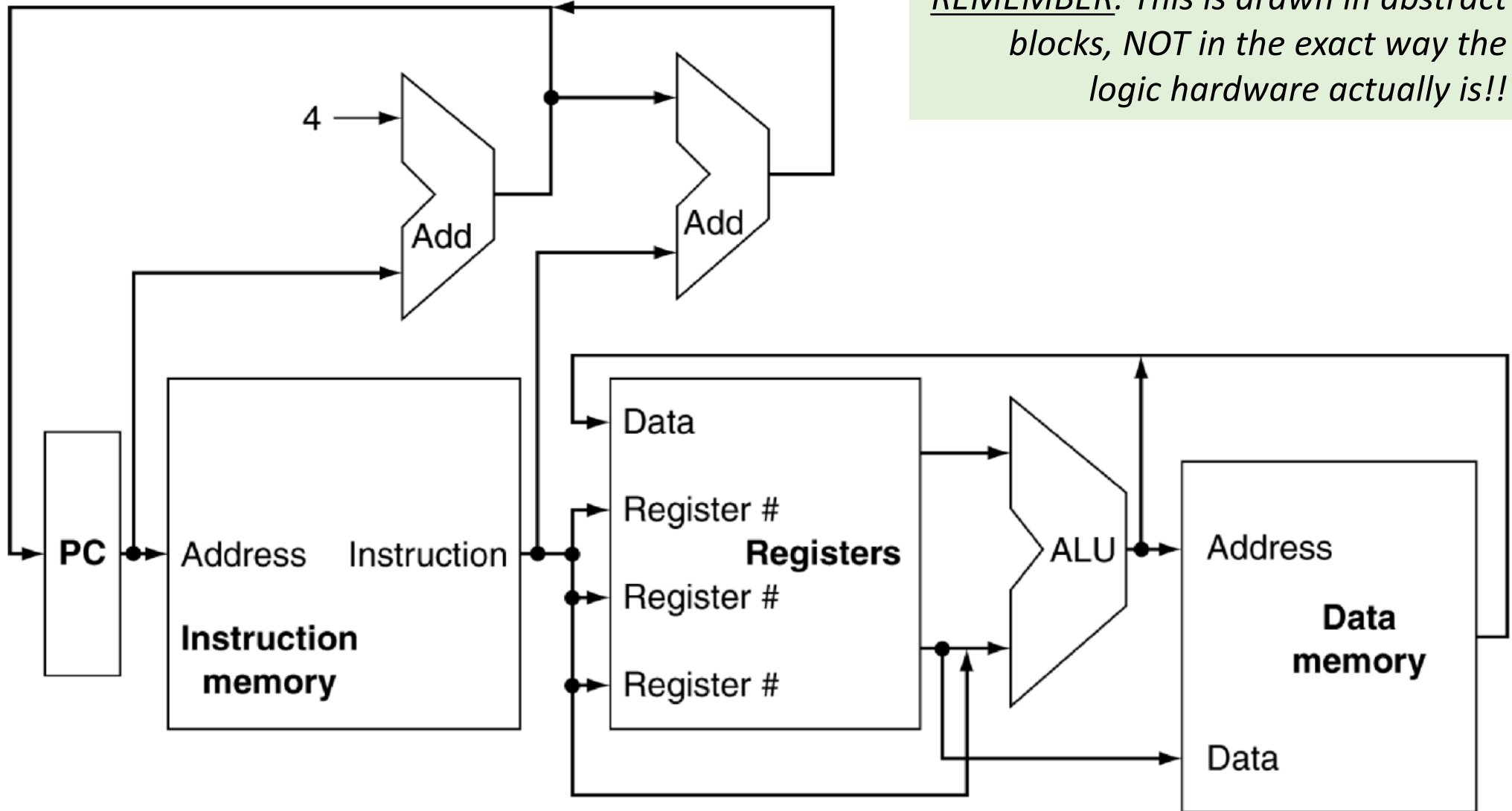General (and Simplified) CPU Hardware Design



Information Encoding

- At the very basic level, an electronic logic circuit has:
 - Input(s) *deal with logic levels of “0” and “1”*
 - Output(s) *and nothing else*
 - Power Supply *it’s how the circuits actually work*
- Power supply (i.e. a battery) voltage range allows for 2 distinct “levels” within that range
 - Low voltage \equiv Logic **0**
 - High voltage \equiv Logic **1**
- One wire per bit
- Multi-bit data encoded on multi-wire “**buses**”

 

The 2 Types of Logic Building Blocks

- **Combinatorial Logic**

- Output is a direct “result” of a combination of inputs
- Input changes mean output changes *immediately**







- **Sequential Logic**

- Output can *optionally*** remain unchanged
- It means that this kind of logic can keep an old output the same *even if the input(s) change(s)!*
- In other words, these circuits have “memory” of “old states”

* In the **physical world**, there is no such thing as “change occurring immediately”.
The use of this term here just means “practically immediately”.



** This means the output must rely on a “special” input to **enable** the output to change.

      Graphical Symbols of Basic Combinatorial Logic Elements





Multiplexers (Muxes)

- Combinatorial circuits who function as a “chooser” between multiple inputs to be “driven to” the output
- Always multiple inputs (N), always ONE output (N-to-1 mux)
 - Can be drawn symbolically in 2 ways (trapezoid vs oval)
--- there’s NO difference, just a preference in drawing
- 1 of the input data lines gets selected to become the output, based on a 3rd “select” (sel) input
 - If **sel** = 0, then I_0 gets to be the output
 - If **sel** = 1, then I_1 gets to be the output
 - So: **OUTPUT** = $I_1 \cdot \text{sel} + I_0 \cdot \overline{\text{sel}}$
- The opposite of a Mux is called a **Demultiplexer** (or **Demux**)

  


ALUs and Adders

  - Combinatorial logic
- ALU takes 2 bus (i.e. multi-bit) inputs and outputs 1 bus, depending on what function (F) is chosen
 - $Y = F(A,B)$
- Adder is really a sub-set of any ALU – we sometimes want to symbolize it separately
 - $Y = A \text{ bit-add } B \text{ (i.e. } A + B)$




Registers

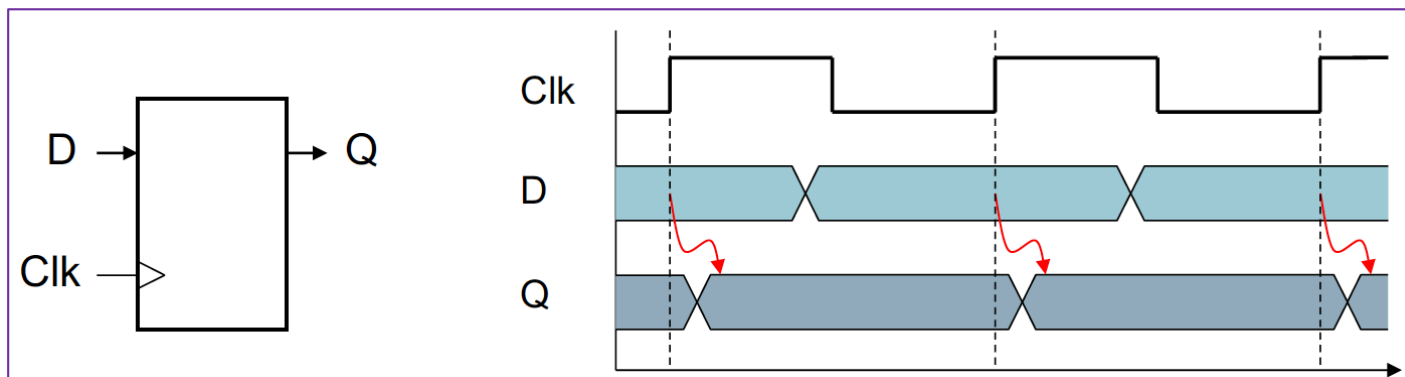- Sequential Logic
- Input passes on to the output **ONLY IF** enabled
 - Otherwise, the output remains in its “old” state
- Typically, registers are D-Flip Flop circuits
 - Uses a **clock signal** to determine when to update the stored value
 - **Edge-triggered**: update when clock signal changes from 0 to 1





Registers with Write Control

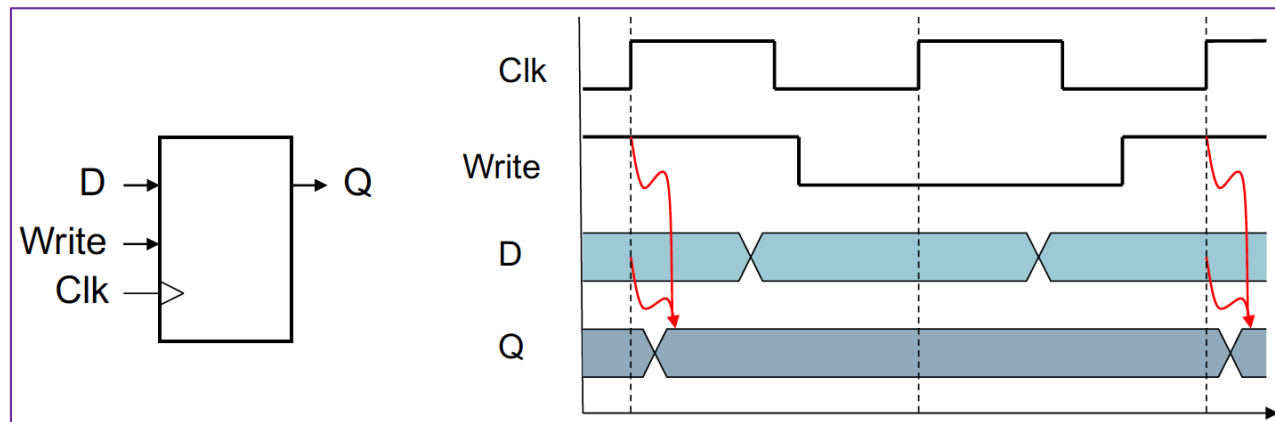- Sometimes registers have an additional enabling mechanism: a WRITE-ENABLE input
- Only updates on clock edge when write-enable control input is 1
- Useful if we don't need to write something right away
 - You can't "mute" the clock signal because it is a global one
 - WRITE-ENABLE is a local signal only to *that particular* register



Clocking Methodology

  
- The same clock signal is propagating to multiple parts of the CPU
- Combinational logic transforms data during clock cycles
 - i.e. *between* clock edges
 - Input from state elements, output to state element
- Longest delay determines clock period
 - Or better said: clock period determines how long the longest delay can be




Building a Datapath

- **Datapath:** Elements that process data and addresses in the CPU
 - Example: Registers, ALUs, muxes, memories, ...
- We will build a MIPS datapath incrementally
 - Refine the overview “simple” design

Simplified CPU Design

 

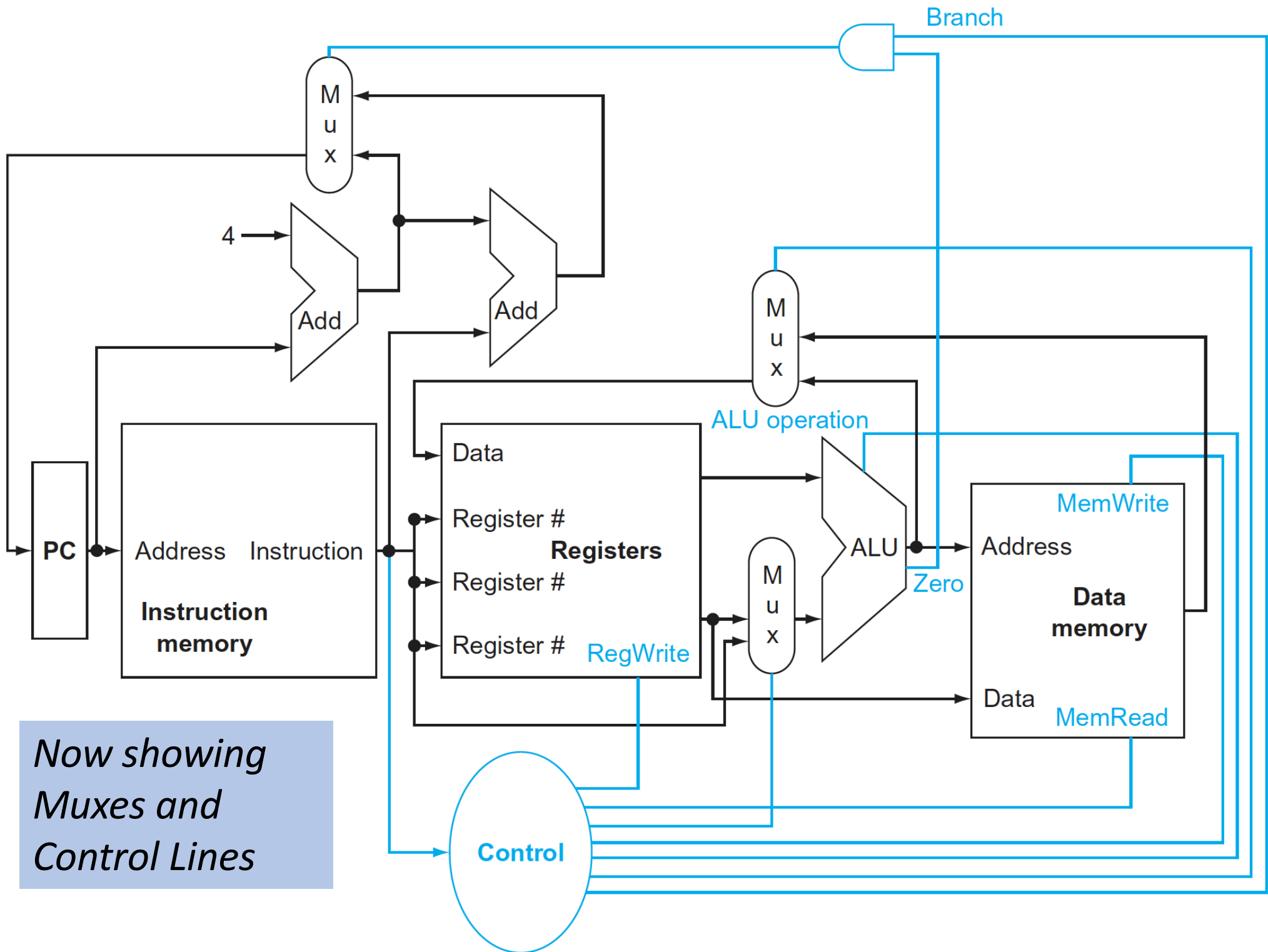


*Now showing
Muxes and
Control Lines*

Ok...

Let's Review it
One Instruction Type at a Time...

First: The Instruction Fetch

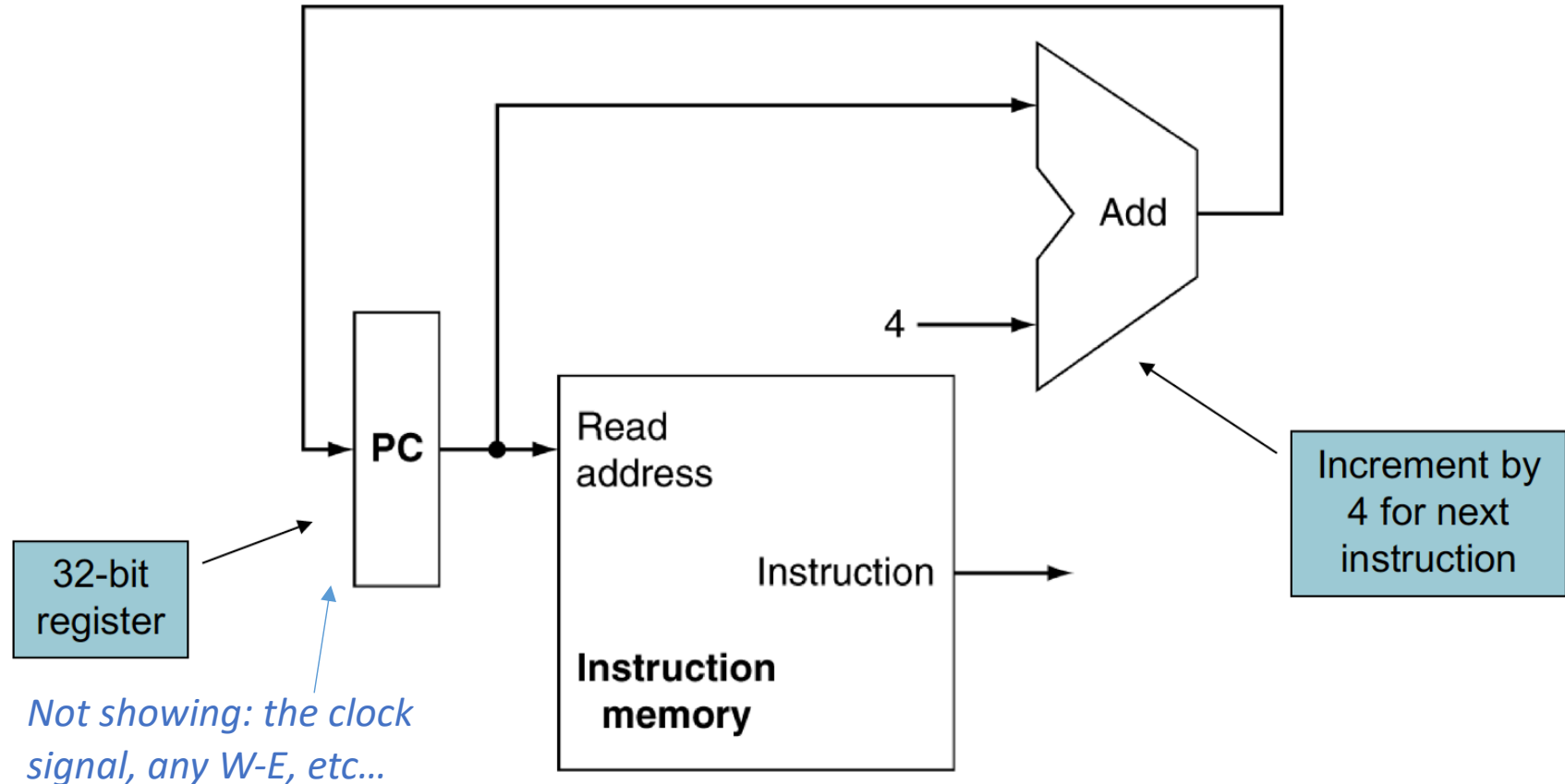


1. To execute **any** instruction, we must start by fetching the instruction from memory.
2. To prepare for executing the *next* instruction, we must also increment the PC so that it points at the next instruction, 4 bytes later.

R-Format Instructions: 3 Steps


- Read **two** register operands (\$rs, \$rt)
- Perform arithmetic/logical operation
- Write register result (\$rd)

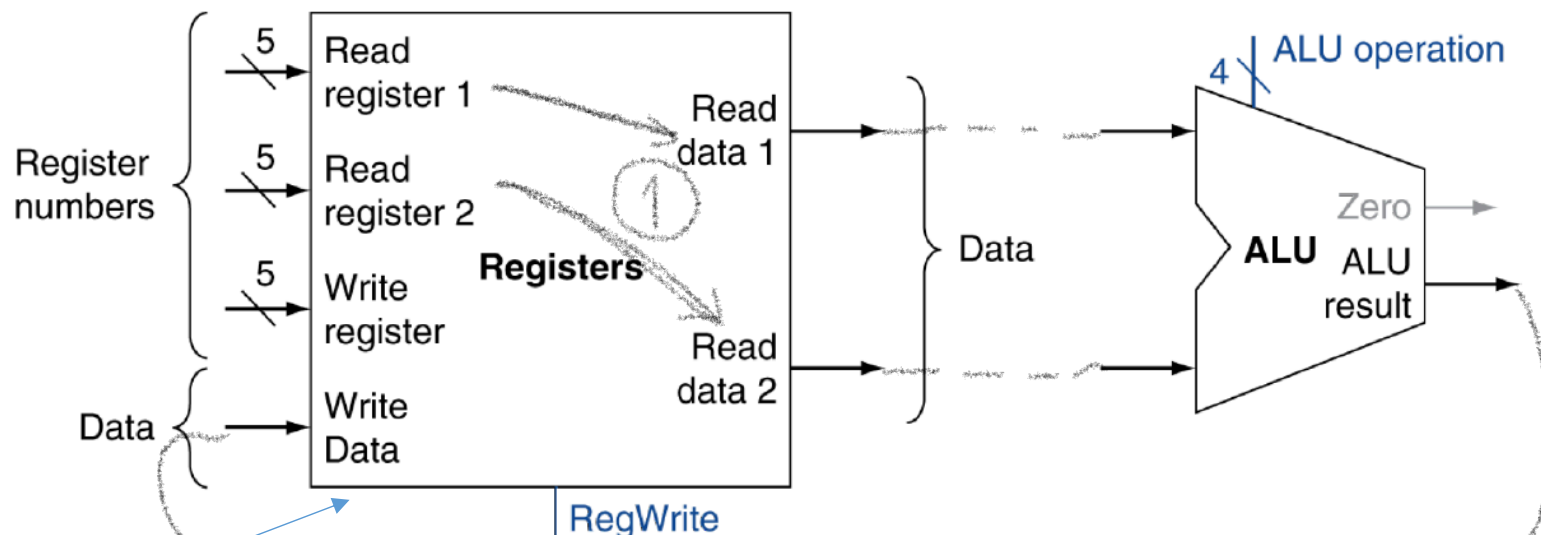*includes add, sub, and, or, slt
e.g.: add \$t1, \$t2, \$t3*




This is the register file

Register File Read and Write

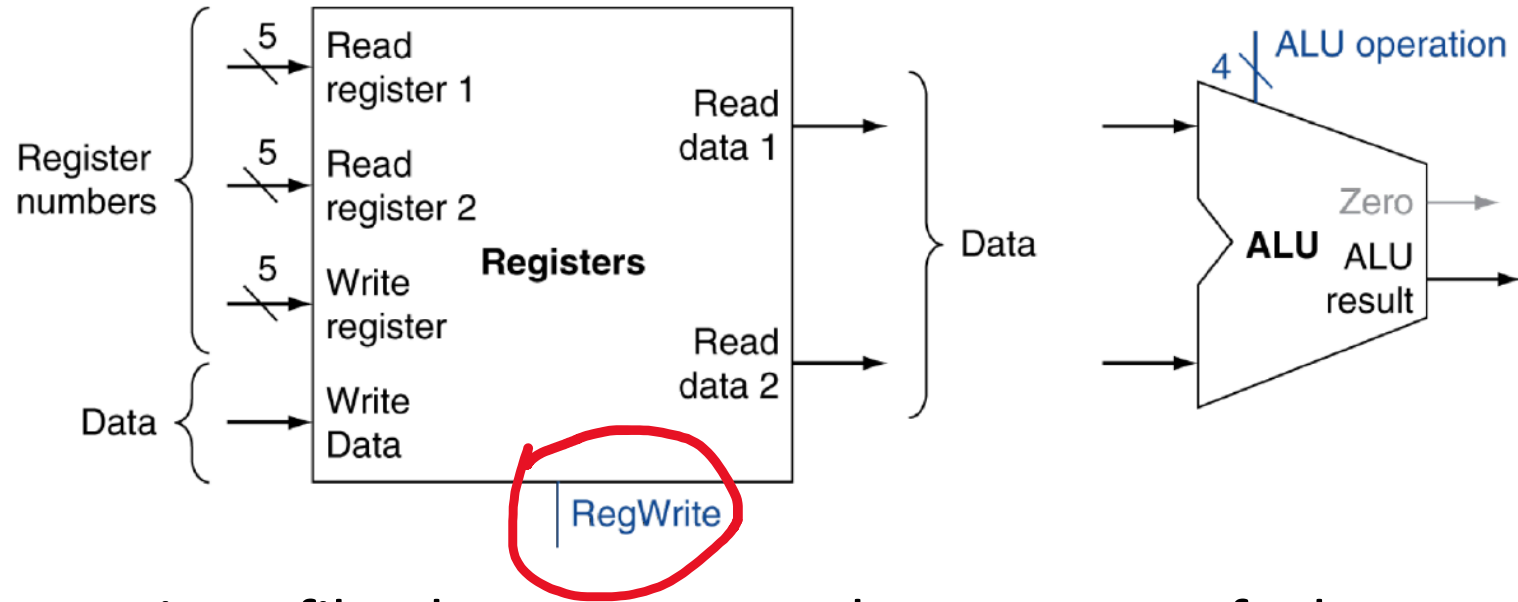

- The register file always outputs the contents of whatever register numbers are on the Read register inputs.
- Writes are controlled by the write control signal, which must be *asserted* for a write to occur at the clock edge.

The ALU Operation

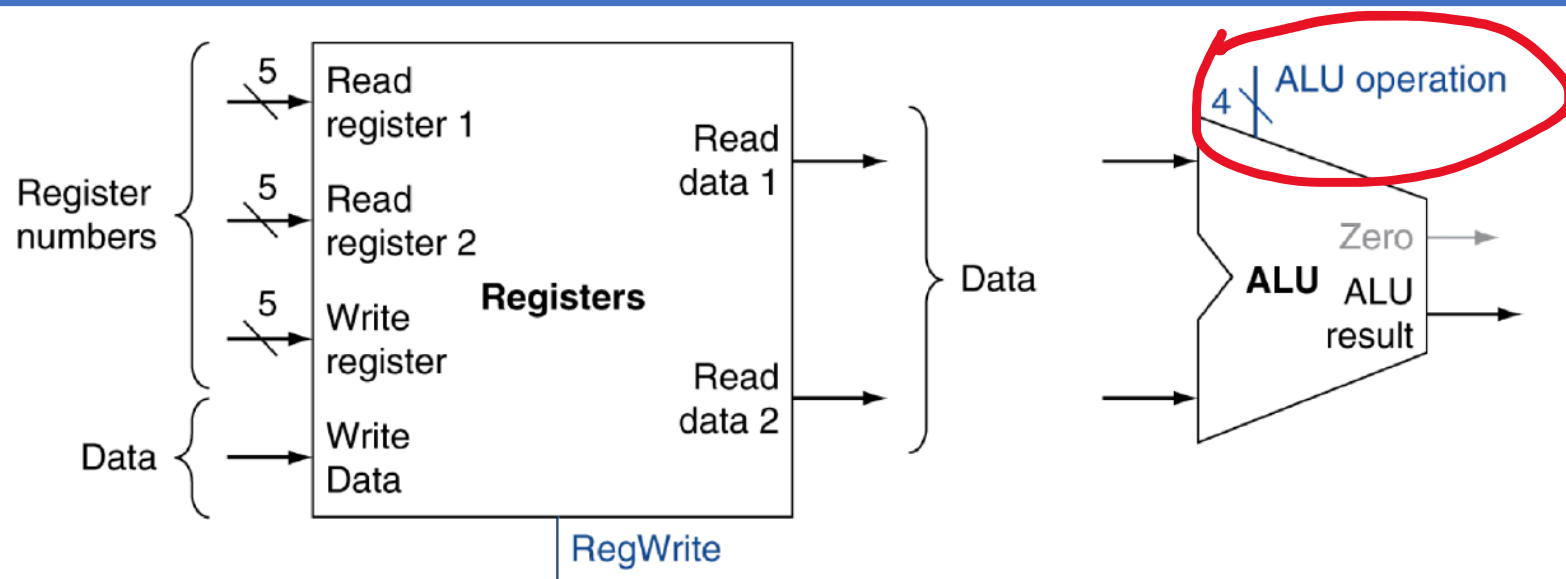


- The ALU takes two 32-bit inputs and produces a 32-bit result
- Also produces a 1-bit signal if the result is 0.
- The 4-bit control signal of the ALU ("ALU operation") tells it what op it's performing on the inputs
 - It's a decoded set of bits... more on those later

Load/Store Instructions


- Read register operands
- Calculate address using 16-bit offset (immediate)
 - First take the offset and sign-extend it to 32-bits
 - Then use ALU
- Load: Read memory and update register
- Store: Write register value to memory

includes lw, sw
e.g.: `Lw $t0, 4($sp)`

We'll also need...

 

a. Data memory unit

 


b. Sign extension unit

Branch Instructions

includes beq, bne
e.g.: beq \$t1, \$t2, Label

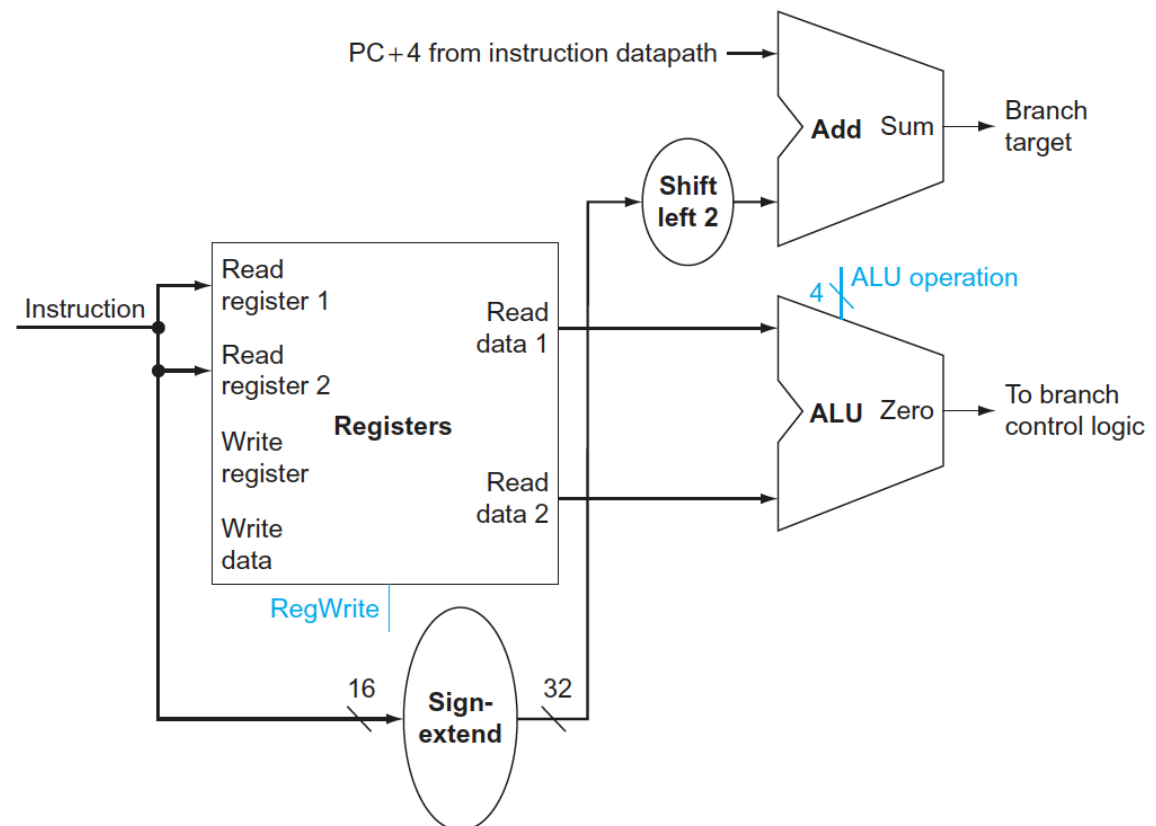- Read register operands
- Compare operands
 - Use ALU, subtract and check Zero output
- Calculate target address
 - Sign-extend displacement
 - Shift left 2 places
 - Add to PC + 4 (already calculated by instruction fetch)



Next Time... Putting them all Together

YOUR TO-DOs for the Week

- Lab 6 will be up soon...
- Assembly programming assignment

</LECTURE>